

Real medical condition called "Anterograde Amnesia"

⊛ Move memento.

A man, suffering from short-term memory loss, uses notes & tattoos to hunt down his wife's killer.

CpE111

Introduction to Computer Engineering

Dr. Minsu Choi

CH 9: Sequential Logic Networks




UNIVERSITY OF MISSOURI-ROLLA
The Name. The Degree. The Difference.

Sequential Logic Networks?

- A sequential logic network is a digital system where the output is determined by both the present input and the result of a previous event.
- Ex) 3-bit counter

 
So, SLN has ability to memorize the previous state.



If count is in range of 0-6, then R=0.
If " 7, then output will reset to 0 on next pulse.

R = 1 if result = 1000 - 1001 - ... - 1111 - 000

 X = Input that causes transition
 R = output




\Rightarrow Symbolic representation of a state

Formal Description of the System: State Diagram

- We define each possible value of the word as a distinct state of the machine.

ex) 3-bit counter

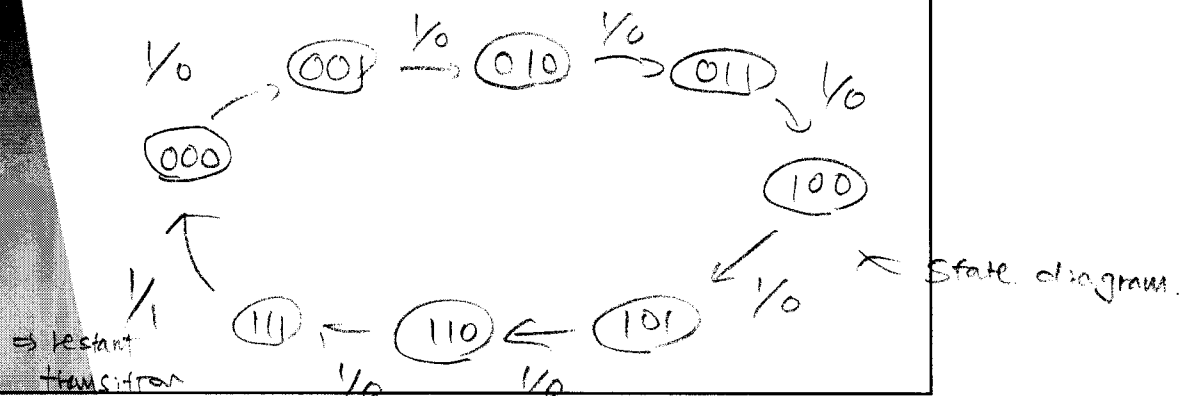


Sequential Network Requirements

- A combinational logic network to perform Boolean operations.
- A memory element that stores the result of an earlier event.
- If we require a clock signal to synchronize the events, it is called "synchronous logic network", also.
- Clocking signal convention: $T = 1$ is assumed.
- $(t-1)$ to t called previous cycle, t to $(t+1)$ called present cycle and $(t+1)$ to $(t+2)$ called next clock cycle.

We now assume that T is the unit clock period

Ex) General Sequential Network #1

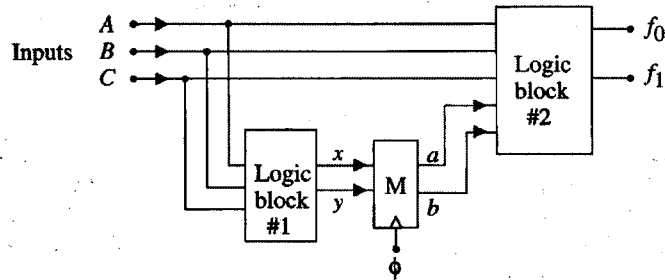

- Two combinational logic blocks #1 and #2 and a state element (a clocked memory) M.


$$a(t) = x(t-1)$$

$$b(t) = y(t-1)$$

$$\Rightarrow f_0 = f_0(A, B, C, a, b)$$


$$f_1 = f_1(A, B, C, a, b)$$

Ex) General Sequential Network #2

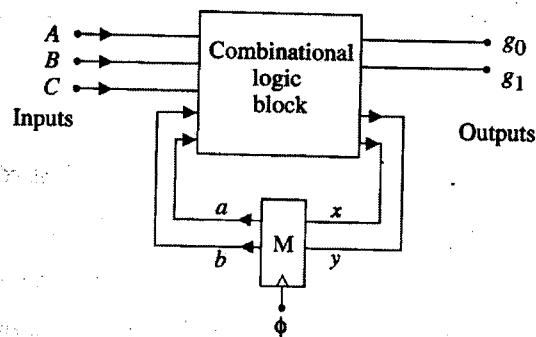

- 1 combinational logic block & 1 memory element and feedback wires.


c/r notation

 


⇒ C acts as a control bit.
 (if $c=0$ then No state change
 if $c=1$ " state change.

Single State Variable Networks

■ Ex1)

 

$$T(t) = C(t) \oplus X(t)$$

 

⇒ circuit diagram.

present value		output	next value
$C(t)$	$X(t)$	$T(t)$	$X(t+1)$
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0


$$X(t+1) = Dx(t) = T(t)$$

⇒ $T(t)$ is used as $X(t+1)$

⇒ state table.

Continued,

■ Ex2)

 



state table:

present state $A(t)$	present inputs $x(t) \ y(t)$		present output $f(t)$	next state $A(t+1)$
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

$$\Rightarrow \begin{cases} f = \overline{x \cdot A + y} \\ D_A = \overline{f} \\ = x \cdot A + y \\ A(t+1) = D_A(t) \end{cases}$$

state diagram.

 

 

$$\Rightarrow g = (U+V) \oplus R$$

$$D_R(t+1) = \overline{U(t) + V(t)} \\ = R(t+1)$$


Continued,

state table

Ex3)

present values				next state
R(t)	U(t)	V(t)	g(t)	R(t+1)
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0


state diagram.

 

Multi-State Variable Networks

- If we have n state variables, then 2^n states are needed when we draw a state diagram.


Ex)

 


present values					next states	
$s(t)$	$x(t)$	$y(t)$	$a_x(t)$	$a_y(t)$	$x(t+1)$	$y(t+1)$
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	1	1	1	1
0	1	1	1	0	1	0
1	0	0	1	1	1	1
1	0	1	1	0	1	0
1	1	0	0	0	0	0
1	1	1	0	1	0	1

$$a_x(t) = S(t) \oplus x(t) \\ a_y(t) = S(t) \oplus x(t) \oplus y(t)$$
 
$$x(t+1) = D_x(t) = a_x(t) \\ y(t+1) = D_y(t) = a_y(t)$$



 

State Diagram to State Table

⇒ For each state, consider outgoing transitions.

Inputs	present state		Next state
X Y	A	B	A B
0 0	0	0	0 0
0 1	0	0	0 1
1 0	0	0	1 1
1 1	0	0	1 0

You need to consider 4 cases since you have 2 input bits.

Sequential Network Design

- We start with a listing of the desired transition characteristics (state table, etc) and use the information to create the network.


- Ex)

single input var $x(t)$
single output var $f(t)$
single state variable $A(t)$
current FF output


present values			next	FF in
$A(t)$	$x(t)$	$A(t)$	$A(t+1)$	$f(A(t))$
0	0	1	1	1
0	1	0	0	0
1	0	1	0	0
1	1	1	1	1

Continued,


K-map to find f & D_A

 

$$f = A + \bar{x}$$


 

 
$$D_A = \bar{A}\bar{x} + Ax = \overline{A \oplus x}$$



Binary Counters

■ Ex) 2-bit counter

  

$$D_0 = \bar{A}_0, D_1 = A_1 \oplus A_0$$

$$A_1(t+1) = D_1(t), A_0(t+1) = D_0(t)$$

present		Next	Inputs to FFs
A_1	A_0	A_1, A_0	D_1, D_0
0	0	0 1	0 1
0	1	1 0	1 0
1	0	1 1	1 1
1	1	0 0	0 0



8 States.

⇒ we need three FFs


Three inputs: D_2, D_1, D_0
 Three outputs: A_2, A_1, A_0

Continued,


■ Ex) 3-bit counter

present $A_2 A_1 A_0$	Next $A_2 A_1 A_0$	Inputs $D_2 D_1 D_0$
0 0 0	0 0 1	
0 0 1	0 1 0	
0 1 0	0 1 1	
0 1 1	1 0 0	→ same
1 0 0	1 0 1	
1 0 1	1 1 0	
1 1 0	1 1 1	
1 1 1	0 0 0	


K-map:

 

D_2 map

 

D_1 map

 

D_0 map.

Continued,


$$D_2 = A_2 \bar{A}_0 + A_2 \bar{A}_1 A_0 + \bar{A}_2 A_1 A_0$$

$$= A_2 \bar{A}_0 + A_0 (A_2 \oplus A_1)$$


$$D_1 = \bar{A}_1 A_0 + A_1 \bar{A}_0 = A_1 \oplus A_0$$

$$D_0 = \bar{A}_0$$

Design

 

 PLA Implementation of 3-Bit Counter (using SOP forms)



$$D_2 = \sum m(3, 4, 5, 6)$$

$$D_1 = \sum m(1, 2, 5, 6)$$

$$D_0 = \sum m(1, 2, 4, 6)$$

Program Completed

University of Missouri-Rolla

© 2003 Curators of University of Missouri

UMR

UNIVERSITY OF MISSOURI-ROLLA
The Name. The Degree. The Difference.