

CpE213 – Digital Systems Design

Homework 1

Ch 1 and Address decoding

NOTE: Just as on tests, I expect you to show all your work on homework problems. A correct answer with no work might not be given full credit.

1. Name 5 important differences between a microcontroller and a microprocessor. What are the *2 most important* differences?
2. For the following circuit:
 - a) What is the address space of RAM1 and ROM1?
 - b) List at least 3 locations that we could address REG1.
3. Say you are trying to hook up RAM (each chip with a standard \overline{CS}) to a microcontroller with 16 address lines (A0 through A15).
 - a) Draw a circuit which uses just 2 74LS138s (and no other parts) to create an address space for 16 4kx8 RAM chips. (Hint: There is a good reason for having multiple chip selects on the 74LS138).
 - b) Extending this model, how would you hook up 74LS138s to create separate address spaces for 8 4kx8 and 16 2kx8 RAM chips (you need only label the pins of the 74LS138s, showing what they would be connected to).
 - c) For part b), find the address space for each chip.