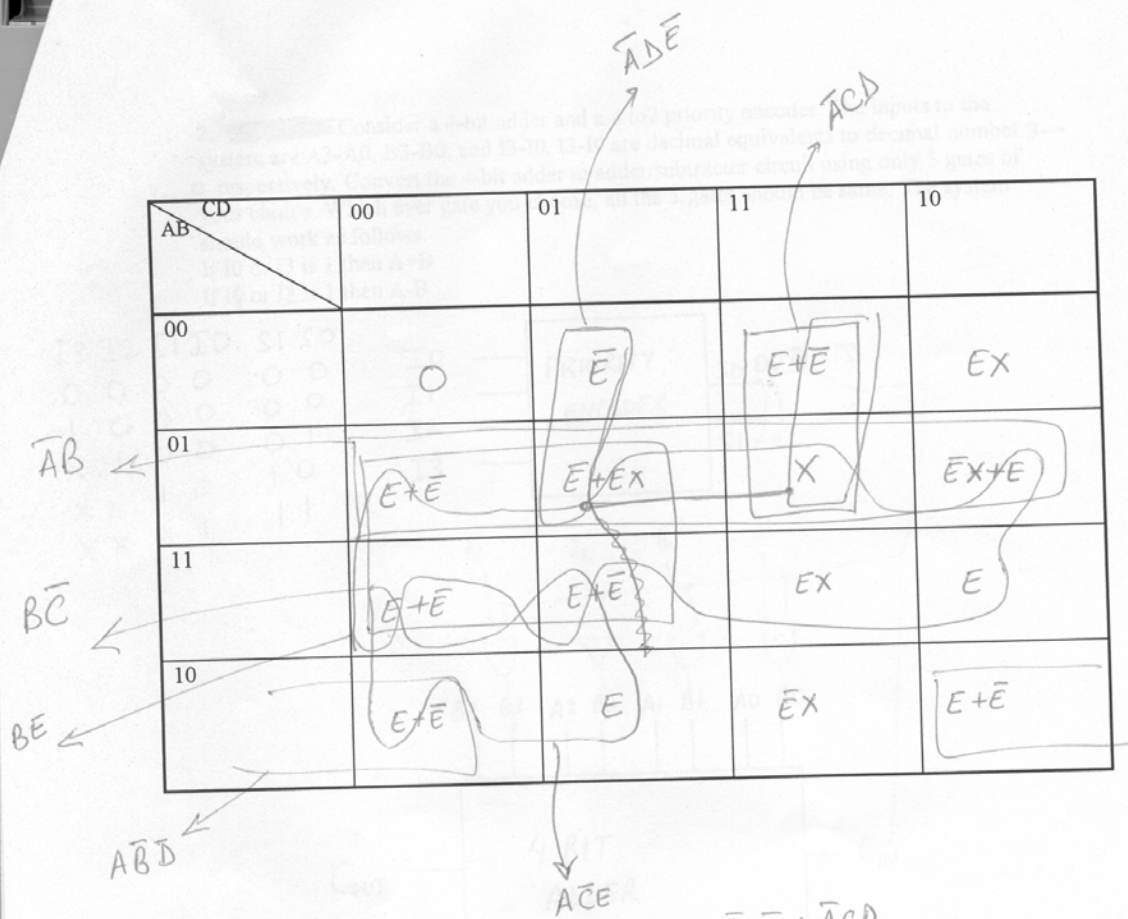


1) Implement the function:

$$F = \Pi M(0, 1, 3, 4, 18, 23, 28, 30) + \Pi M_x(5, 11, 12, 14, 15, 22, 31)$$


Fill in the truth table. Implement the function using 16:1 MUX and also get the minimal SOP equation using the k-map on the next page.

Decimal	ABCDE	F	F(E)
0	00000	0	0
1	00001	0	0
2	00010	1	\bar{E}
3	00011	0	\bar{E}
4	00100	0	
5	00101	X	EX
6	00110	1	$E + \bar{E}$
7	00111	1	$E + \bar{E}$
8	01000	1	$E + \bar{E}$
9	01001	1	$E + \bar{E}$
10	01010	1	$\bar{E} + EX$
11	01011	X	
12	01100	X	$\bar{E}X + E$
13	01101	1	
14	01110	X	X
15	01111	X	
16	10000	1	$E + \bar{E}$
17	10001	1	$E + \bar{E}$
18	10010	0	E
19	10011	1	E
20	10100	1	$E + \bar{E}$
21	10101	1	$E + \bar{E}$
22	10110	X	$\bar{E}X$
23	10111	0	
24	11000	1	$E + \bar{E}$
25	11001	1	$E + \bar{E}$
26	11010	1	$E + \bar{E}$
27	11011	1	$E + \bar{E}$
28	11100	0	E
29	11101	1	E
30	11110	0	E
31	11111	X	EX




$$SOP = \bar{A}\bar{C}E + \bar{A}\bar{B}\bar{D} + BE + B\bar{C} + \bar{A}\bar{B} + \bar{A}\bar{D}\bar{E} + \bar{A}CD$$

$$X = D$$

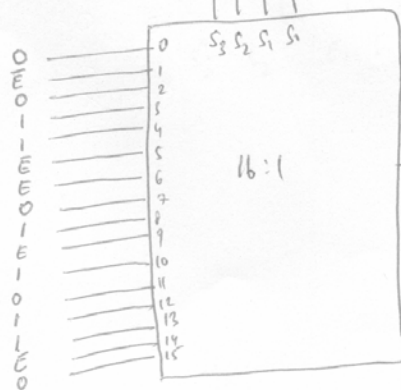


2. Consider a 4-bit adder and a 4 to 2 priority encoder. The inputs to the system are A_3-A_0 , B_3-B_0 , and I_3-I_0 . I_3-I_0 are decimal equivalents to decimal number 3 respectively. Convert the 4-bit adder to adder/subtractor circuit using only 5 gates of your choice. Which ever gate you choose, all the 5 gates should be same. The system should work as follows.
 If I_0 or I_3 is 1 then $A+B$
 If I_1 or I_2 is 1 then $A-B$

I_3	I_2	I_1	I_0	S_1	S_0
0	0	0	0	0	0
1	0	0	0	0	0
x	1	0	0	0	1
x	x	1	0	1	0
x	x	x	1	1	1

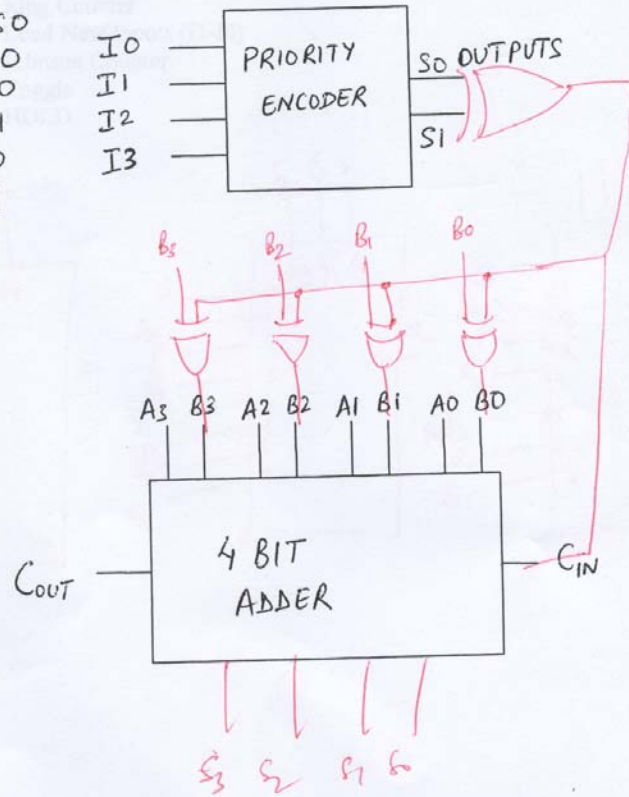

3) Design and draw a 4-bit universal shift register application using only multiplexers.
The system should function according to the following function table. The outputs of the shift register is Q3-Q0

S2	S1	S0	Function
0	0	0	Shift Left
0	0	1	Shift Right
0	1	0	Set
0	1	1	Ring Counter
1	0	0	Load New Inputs (I3-I0)
1	0	1	Johnson Counter
1	1	0	Toggle
1	1	1	HOLD

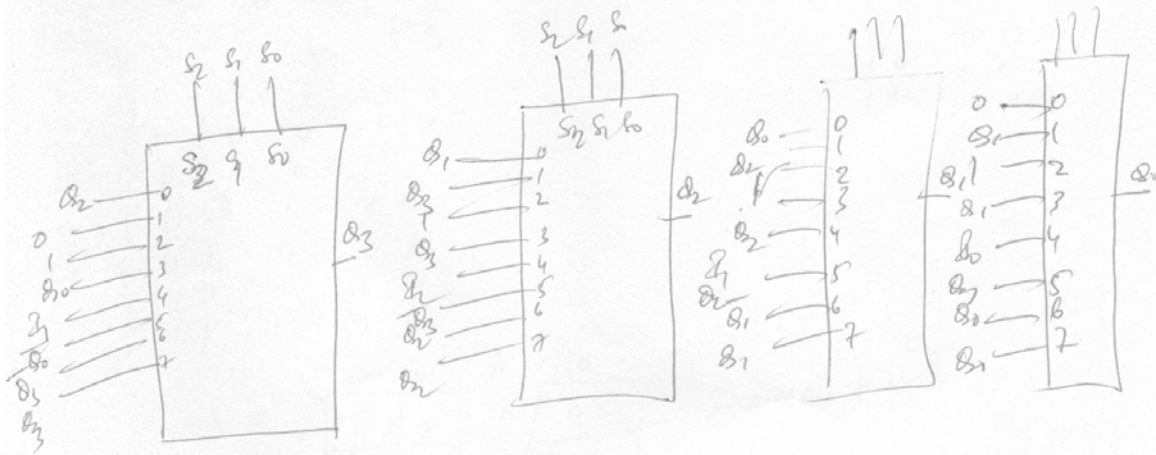

4) Design a flip-flop with the below given truth table using a S-R flip-flop.

U	V	Output
0	0	SET
0	1	RESET
1	0	TOGGLE
1	1	SET

NAME _____

U	V	Q_0	\bar{Q}_0	S	R
0	0	0	1	1	0
0	0	1	0	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	0	0	1
1	1	0	1	1	0
1	1	1	0	X	0

S R Q_0 \bar{Q}_0

00, Hold

01 0 1

10 1 0

11 NOT USED

$S = \bar{U} \bar{V} Q_0 + U \bar{V} \bar{Q}_0$

$\bar{U} \bar{V}$	Q_0	\bar{Q}_0
00	1	0
01	X	1
11	0	X
10	0	1

$R = U \bar{V} Q_0 + \bar{U} V \bar{Q}_0$

$U \bar{V}$	Q_0	\bar{Q}_0
00	0	0
01	0	1
11	1	0
10	0	0

