

CpE111

Introduction to Computer Engineering

Dr. Minsu Choi
CH 4: Digital Hardware




UNIVERSITY OF MISSOURI-ROLLA
The Name. The Degree. The Difference.

Hardware?

- The physical realization of a digital element or system.
- How to represent logic 0 and logic 1 states?
 1. Voltage V , which has units of volts (v).
 2. Electrical current I , which has units of ampres (A or amps).
- Two are related: a voltage causes electrical current to flow.
- Most digital logic chips use two different voltage ranges to define logic 0 and logic 1 conditions.

Power Supply

 - All electronic networks require a power supply to operate.
- In digital circuits, the power supply is usually modeled as a voltage source with a value that we will denote by V_{DD} (usually 5v, 3.3v or 2.5v).
- Ex) schematic diagram of a digital system with a power supply (since the drawing shows the "scheme" used to construct the circuit).




positive side voltage is higher as much as V_{DD} volts

← Ground is at 0v.


Logic Levels

 - Logic 0 \rightarrow 0v and Logic 1 \rightarrow V_{DD} (ex., 5v), in general.
- Low voltage represents logic 0 & high voltage represents 1 \rightarrow called positive logic.
- High voltage represents logic 0 & low voltage represents 1 \rightarrow called negative logic.
- Two voltage ranges are used in practice.




Digital Integrated Circuits

 - ICs (Integrated Circuits) = Computer chips.
- Dual inline package (DIP) is very common packaging technology for computer chips.



 - To build more complex digital systems -> use PCB (Printed Circuit Board).




Silicon chip inside

=> complex circuit is fabricated on a silicon chip by optical lithography.

Pin-Out Diagram

 
- The logic functions that a particular chip implements are usually shown by embedding equivalent logic diagrams in package outline drawings.
- Ex) Quad-AND chip. V_{CC} is an alternative notation for the power supply voltage.



$$\text{ex) } p_{m3} = p_{m1} \cdot p_{m2}$$

Different Packaging Technologies?

 - PGA (Pin Grid Array) is used for most microprocessor chips, since larger chip can be embedded and larger # of pins can be allocated.
- There are different variations – INTEL's LGA775 and AMD's Socket939.



ICs can be categorized with respect to the # of gates inside


IC Integration Levels

- SSI (Small-Scale Integration): ICs with a few gates.
- MSI (Medium-Scale Integration): ICs with a few hundred gates.
- LSI (Large-Scale Integration): 1K – 100K gates.
- VLSI (Very Large-Scale Integration): a few million gates.
- ULSI (Ultra Large-Scale Integration): around one billion gates.
- Ex) INTEL Pentium 4 processor has about 125 million gates.


Logic Delay Times

- Waveform (a plot of a variable as a function of time) is used to measure the behavior of a gate.

- Ex)

 

(a) Logic gate

 

(b) Ideal waveforms

→ input waveform

→ output waveform


- In the real world, a voltage cannot change instantaneously.

⇒ There should be some delays for $0 \rightarrow 1$ & $1 \rightarrow 0$ transitions


Output Switching Times

- Two time intervals must be considered:

 - t_{LH} , the output low-to-high time, also called the rise time, t_r .
- t_{HL} , the output high-to-low time, also called the fall time, t_f .
- By convention, these time intervals are not measured between 0v to V_{DD} , but represent the transition required between 10% to 90% voltage levels, as shown below.



(a) Logic gate

 

(b) Low-to-high and high-to-low times

Continued,

- The minimum amount of time needed for the gate to switch from 0 to 1 then back again is given by:

$$t_{min} = t_{LH} + t_{HL}$$

- The maximum switching frequency is:

$$f_{max} = \frac{1}{(t_{LH} + t_{HL})} \text{ [in Hz]}$$

- = max # of logic transitions that the gate can make in 1 sec.

- Ex) $t_{LH} = 7.2 \text{ ns}$ & $t_{HL} = 3.9 \text{ ns}$, $f_{max}?$



$$f_{max} = \frac{1}{7.2 \times 10^{-9} + 3.9 \times 10^{-9}} = 90.09 \text{ MHz}$$

(≈ 90.09 million transitions per sec max)

Propagation Delay

- It can be hard to keep track of both delay times for every logic gate.
- At the logic design level, it is simpler to introduce a single delay time that represents an average switching time, called “propagation delay”, from the input to the output.
- This is to include the physical delay of a logic signal as it “propagates” through a chain of gates.

Inverter Gate Example

  

- Then, t_p (=propagation delay) = $1/2 (t_{PHL} + t_{PLH})$ or $=\max(t_{PHL}, t_{PLH})$, alternatively.

Fan-In & Fan-Out


- The fan-in of a digital logic gate refers to the number of inputs.
- Ex) inverter has fan-in of 1 and NAND2 has fan-in of 2.
- The fan-in provides information about intrinsic speed of the gate -> the propagation delay increases with the fan-in.
- Ex) OR2 is faster than OR3.

Continued,

- The switching time of an electronic gate depends on the number of gates that are driven (or connected) at the output.
- The fan-out of a gate is the number of gates that are driven by the output, and it depends how the gate is used in the logic chain -> increasing the fan-out slows down the logic flow through the gate.
- If no additional gate -> no load (fan-out=0)

Ex) $A \xrightarrow{t_{p0}} \neg A$ no load propagation delay.


- Fan-out=1 ->

 

$$t_{p1} = t_{p0} + 1 \cdot t_{PL}$$

additional delay time needed to drive the load (next inverter).


- Fan-out=N ->

 

$$t_{pN} = t_{p0} + N \cdot t_{PL}$$

Logic Cascades and Delays

- Ex) linear chain of 4 inverters.

 

$$t_d = t_{d1} + t_{d2} + t_{d3} + t_{d4}$$

Fan-in & fan-out delays must be considered.


$$t_{d4} = \underbrace{t_{to, NOT}}_{\text{no-load P.D.}} + t_L$$

The load at the forth gate is not specified. So, t_L is used.

$$t_d = \underbrace{4 \cdot t_{to, NOT}}_{\text{no-load prop delay}} + \underbrace{3 t_{PL NOT}}_{\text{fan-out delay}} + t_L$$

Continued,

 
- Ex) Inverter chain with increased internal delay.



$$t'_d = \underbrace{4 \cdot t_{p0, \text{NOT}}}_{\substack{\text{no-load} \\ \text{prop delay}}} + \underbrace{6 \cdot t_{pL, \text{NOT}}}_{\substack{\text{6 fan-outs} \\ \text{driven}}} + t_L$$

⇒ takes more time because of more fan outs!

Basic Electric Circuits

 


- Let's consider electric current flowing through a wire.
- The current I (measured in amperes, A) represents the flow of charge (denoted by Q , measured in units of coulombs, C) across a reference area shown.
- So, the current is the time rate of change of the charge across the area, as given by the derivative; $I = dQ/dt$.
- $1A = 1C/sec$ crossing the reference plane.
- Electrons flow right to left and current flows in the direction of positive charge (left to right).
- The voltage on the left side is higher than the right side.


Resistance

Resistance

 
- Every electronic device has a natural tendency to "resist" the flow of charge -> Resistance (parameter R is used).
- $R = V/I$
 voltage
 current
- The unit of resistance is the ohm (Ω).
- Ex) 1Ω resistor admits 1A of current with 1v applied across it -> Ohm's law.



(a) General device

 

(b) Resistor symbol

 

(c) Current vs. voltage

$$V = IR \Rightarrow I = V/R = \frac{1}{R} \cdot V$$

slope

=> Linear relationship between I & V .

Power Dissipation (P) of Resistor

- The power dissipation of a resistor in units of watts (W) is given by:
- $P = VI = (IR)I = I^2R$ (since $V = IR$, Ohm's law).
- Ex) Power dissipation of a resistor at 15v and 5A.


$$R = V/I = 15/5 = 3\Omega$$

$$\text{so, } P = (5A)^2 \cdot 3\Omega$$


$$= 25 \times 3 = 75 \text{ Watts.}$$

Capacitance

 
- A parameter that describes how a particular device can store electric charge.
- Ex) Parallel-plate capacitor.



(a) Structure

 

(b) Circuit symbol

 

(c) Charge vs. voltage

Continued,

- The device consists of two metal plates that are separated from each other by an insulating layer such as glass.
 1. A voltage V is applied to the plates as shown.
 2. A charge of $+Q$ is induced on the top plate and a charge of $-Q$ is induced on the bottom plate.
 3. Then, the amount of charge Q stored is $Q = CV$.
- The unit of capacitance is the farad (F) such that $C = Q/V$.

ex) charge 10C & 5V, capacitance?


$$C = \frac{10C}{5V} = 2F$$

charge
unit: coulomb.
→ voltage
capacitance

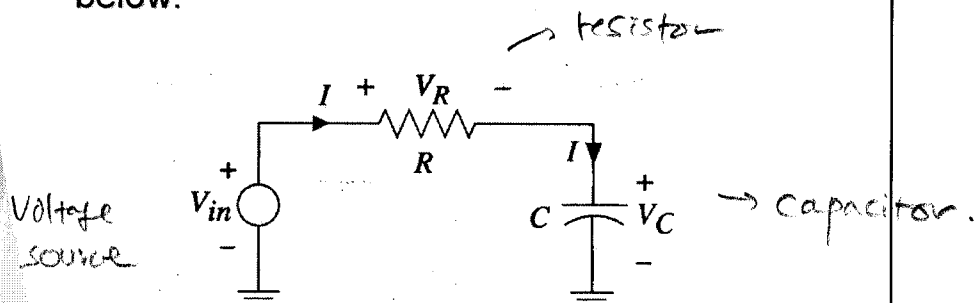Examples

The RC (Resistor-Capacitor) Circuit


- Digital switching networks are often modeled by using the series-connected RC circuit shown below.



Continued,

1. Three components carry the same current I , since they are connected in series.
2. But three different voltages are shown; V_{in} (input voltage), V_R (resistor voltage) and V_C (capacitor voltage).
3. The relationship among these voltages is from Kirchhoff's voltage law (KVL);
 - Sum of voltage rises = sum of voltage drops.
 - $V_{in} = V_R + V_C$
 - So, V_R & V_C respond to changes in the input voltage V_{in} .


RC Circuit Behavior

 

- Input voltage $V_{in}(t)$ from 0V to a high voltage V_H at time t_1 and then back to 0V at time t_2 .
- Then, capacitor voltage $V_C(t)$?

Continued, V_H

- When V_{in} is charged to a high voltage V_H , current starts flowing. The current is given by: $I = dQ/dt$ (current is the time rate of change of the charge).
- So, the current "charges the capacitor" and the capacitor charge Q_C increases with time; $V_C = Q_C/C$.
- When input voltage switches back down to 0v, V_C decays to 0v.
- $\rightarrow Q_C$ goes up, then V_C goes up; Q_C goes down, then V_C goes down with time.

 

Capacitor charge
(increase with time).

$$V_C = \frac{Q_C}{C}$$

↓
C stays.

Detailed Analysis

- The time delay as the capacitor voltage changes from 0 to V_H is due to the resistance R in the circuit, which impedes the current flow.

$$\rightarrow V_R = IR$$

$$\rightarrow V_R = V_{in} - V_C \text{ (by KVL)}$$

$$\text{So, } I = (V_{in} - V_C)/R$$

- When the capacitor is charged, the voltage increases according to the formula:

$$V_C(t) = V_H [1 - e^{-(t-t_1)/\tau}] \quad t \geq t_1$$

\rightarrow "a.u."

- \rightarrow exponential dependence formula: (e is "Euler e" and $e = 2.71828...$ and τ (tau) is called the time constant and $\tau = RC$ seconds).

Continued,

- τ represents the delay for the capacitor voltage to change from 0v to a certain high level that is chosen at time τ seconds from t_1 .
- -> The voltage at this time is...

$$V_C(t = t_1 + \tau) = V_H [1 - e^{-1}] = 0.632 V_H \approx (2/3) V_H$$


- Small τ means fast transition.
- Large τ means slow transition.

Continued,

- The discharge event is similar:

$$V_C(t) = V_H e^{-(t-t_2)/\tau} \quad t \geq t_2$$
 
$$V_C(t = t_2 + \tau) = V_H e^{-1} = 0.368 V_H \approx (1/3) V_H$$



$$V_H \rightarrow V_C = (0.3/5) \cdot 5V = 1.84V$$

also takes 1ns.

Example

- Consider an RC circuit with values of $R=1000\Omega$ and $C=10^{-12}F$.

So, $\tau = RC = 10^3 \times 10^{-12} = 10^{-9} \text{ sec} = 1\text{ns}$.
 If $V_H = 5V$, then a low-to-high transition from 0V to $V_C =$
 $(1 - 0.32) \cdot 5V = 3.16V$ takes $\tau = 1\text{ns}$.

- What if we reduce $R = R=1000\Omega$ to 500Ω and $C=5^{-12}F$?
 $\tau = 500 \times 5 \times 10^{-13} = 0.25\text{ns}$.

\Rightarrow 4 times faster transitions.

- Keeping $R=1000\Omega$, how can we achieve $\tau=0.25\text{ns}$?

$$RC = 0.25\text{ns}$$


$$\Rightarrow 1000 \times C = 0.25\text{ns} \Rightarrow C = 2.5 \times 10^{-13} F.$$

Application to Digital Circuits


- Transitions 0 \rightarrow 1 and 1 \rightarrow 0 take time.
- The switching time of every digital electronic network is governed by any resistance and capacitance in the network.
- Parasitic elements: unwanted resistance and capacitance contributions that cannot be eliminated and that act to slow down the network response.
- So, keeping R and C as small as possible is desired!

Transmission Lines

 - Another type of logic delay arises when we analyze the physics of transmitting a voltage along a wire.



 - Transmission line signal delay ($= t_s$) + the voltage at the end of transmission line takes time to "build up" to the final value $= t_d$.



Program Completed

University of Missouri-Rolla

© 2003 Curators of University of Missouri



UNIVERSITY OF MISSOURI-ROLLA
The Name. The Degree. The Difference.