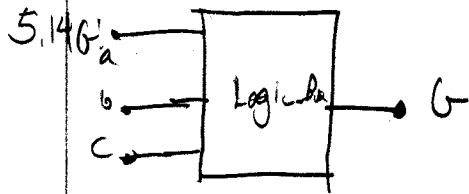


9.0

CpE 111- HW 06

5.14, 5.17, 6.1(b), 6.2(b), 6.3(b)

Jess Law  
10/13/99



table

$$\Sigma H = 57.0$$

$$\Sigma M = 143.0$$

entity logic-box is  
 port (a, b, c : in bit;  
       G : out bit);

end logic-box;

architecture dataflow of logic-box is  
 begin G <= '0' when a='0' and b='0' and c='0' else  
       '0' when a='0' and b='1' and c='1' else  
       '1';  
 end dataflow;

5.17 entity problem-5-17 is  
 port (A, B: in bit-vector (3 downto 0));  
 compare: out (bit);  
 end problem-5-17;

architecture dataflow of problem-5-17 is  
 begin


compare <= '1' when A(3) = B(3) else  
 '1' when A(2) = not B(2) else  
 '1' when A(1) = B(1) else  
 '1' when A(0) = not B(0) else  
 '0';

and  
 not or


end dataflow;

$V_{DD}$   
 0


6.1 (b)

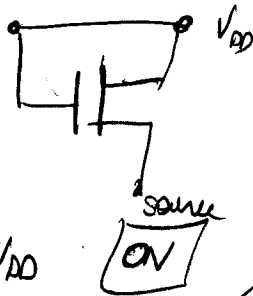

6.2 (b)

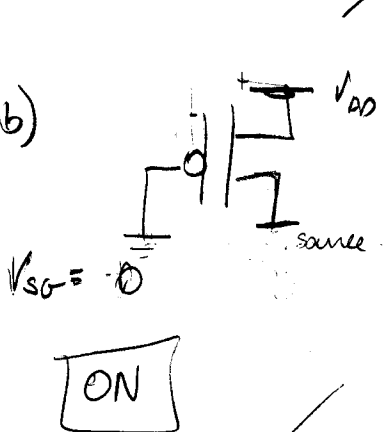

6.3 b) 6:  $\bar{x}$

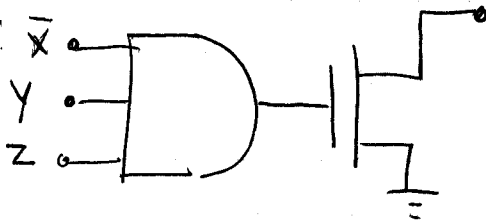

x	y	z	$\bar{x}$	$\bar{x}yz$
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

$x = 0; y = 1; z = 1$