 


10

CpE 111 - Chapter 5: HWs ✓
 5.2, 5.3, 5.6, 5.9, 5.12

Jesse Lai
 10/6/09

5.2 G: diagram & TT
 F: VHDL entity & architecture
 S:



a	b	g
0	0	0
0	1	1
1	0	1
1	1	0

$$a \oplus b$$

entity Excl-2 is
 port (a, b: in bit;
 g: out bit);
end Excl-2;

architecture Internal of Excl-2 is
 begin
 g <= a xor b;
end Internal;

5.3 G: $g = a \cdot b + c \cdot d$
F: VHDL statement using concurrent operations
S:

$$g \leftarrow (a \text{ and } b) \text{ or } (c \text{ and } d);$$

5.6 G: $f \leftarrow (a \text{ and } b) \text{ or } (c \text{ and } (w \text{ xor } z))$;
F: simplest boolean equation
S:

$$f = a \cdot b + (c \cdot (w \oplus z))$$

$$w \oplus z = w \cdot \bar{z} + \bar{w} \cdot z$$

$$c \cdot w \oplus z = c w \bar{z} + c \bar{w} z$$

$$f = ab + c w \bar{z} + c \bar{w} z$$

5.9 PD Diagram

F: VHDL listing that describes circuit

S: entity Logic-circuit is

port (a, b, c, d, e : in bit;

 Detect : out bit);

architecture Basic of Logic-circuit is

begin
 Detect <= ((a and b) or c) nand (d or e);
end Basic;

5.12 G: diagram

F: VHDL listing using vector statements

entity Logic-box is

port (a, b : in bit-vector (3 downto 0);

 Out-1, Out-2 : out bit);

end Logic-box;

architecture Basic of Logic-box is

begin

 Out-1 <= (a(3) xor b(3)) and (a(2) and b(2));

 Out-2 <= (a(1) or b(1)) or (a(0) and b(0));

end Basic;