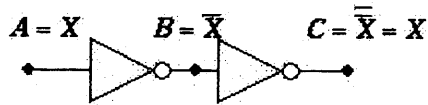


Chapter 2 Boolean Algebra and Logic Gates

[2.1]



A = X	B = \bar{X}	C = $\bar{\bar{X}} = X$
0	1	0
1	0	1

[2.2]



a	b	c	F(a,b,c)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

[2.3]




a	b	c	F(a,b,c)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

[2.4] $f = \overline{a + b}$




a	b	f
0	0	0
0	1	1
1	0	0
1	1	0

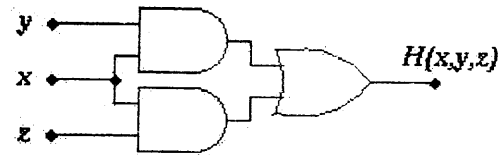[2.5] $H(x,y,z) = x \bullet y + x \bullet z$




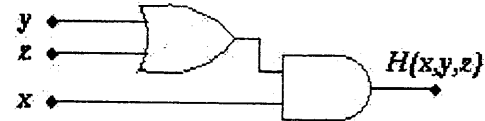The following simplification can reduce the number of gates required for the same function:
 $H(x,y,z) = x \bullet y + x \bullet z = x \bullet (y + z)$



[2.6] Same as 2.5 by replacing w(a,b,c) for H(x,y,z), b for x, and a and c for y and z respectively.

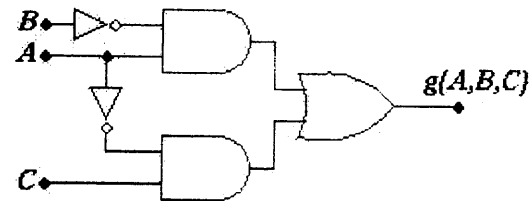[2.7] $g(A,B,C) = A \bullet \bar{B} + C \bullet \bar{A}$



[2.8] $f = \overline{(a + b)} = a \bullet \bar{b}$

[2.9] $g = \overline{((x \bullet y) + z)} = (x \bullet y) \bullet \bar{z} = x \bullet y \bullet \bar{z}$

[2.10]

$$f_1 = \overline{(u \bullet w)} = u + \bar{w}$$

$$f_2 = u + v$$

[2.11]

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0


From the truth table above, F can be simplified as follow:

$$\begin{aligned}
 F &= \bar{A} \bullet B + A \bullet \bar{B} + \bar{A} \bullet \bar{B} \\
 &= \bar{A} \bullet B + (A + \bar{A}) \bullet \bar{B} \\
 &= \bar{A} \bullet B + \bar{B} \\
 &= \bar{A} + \bar{B} = \overline{(A \bullet B)}
 \end{aligned}$$


[2.12] $T(a,b,c) = a \bullet b + \bar{b} \bullet (a + c)$

a	b	c	T(a,b,c)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

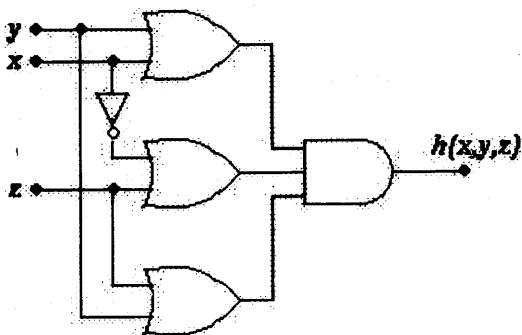[2.13] $h(x,y,z) = (x + y) \bullet (\bar{x} + z) \bullet (y + z)$



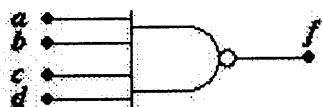[2.14] A 4-input NAND gate is shown below:



If (any one of the inputs is 0)
then

$$f = 1$$

else

$$f = 0$$

[2.15] A 4-input NOR gate is shown below:



If (any one of the inputs is 1)
then

$$f = 0$$

else

$$f = 1$$

[2.16] If ($\phi = 1$)

then

$$f = a \bullet b$$

else if

($\phi = 0$)

then

$$f = 0$$

The output, f , only depends on the inputs when the clock signal ϕ is 1.

[2.17] $Q = x \bullet y + z$

x	y	z	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

[2.18] $h = a \bullet b + \bar{a} \bullet b$

a	b	h
0	0	0
0	1	1
1	0	0
1	1	1

$$h = a \bullet b + \bar{a} \bullet b = (a + \bar{a}) \bullet b = 1 \bullet b = b$$

The function h can be simplified as shown above using the **complementary property**,

$$a + \bar{a} = 1$$

[2.19] $F = \bar{A} \bullet B + A \bullet \bar{B} \bullet C$

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

The above function is at the simplest form.
Thus, no simplification is possible.

$$[2.20] \quad F = \overline{A \cdot B + (A \cdot B) \cdot C} = (\overline{A \cdot B + A \cdot \overline{B} + C}) \\ = (\overline{A \cdot B} + \overline{C}) = \overline{A} \cdot \overline{B} + \overline{C}$$

$$[2.21] \quad F = (X + \overline{Y}) \cdot (X + Y) \cdot Z = (X + (\overline{Y} \cdot Y)) \cdot Z = X \cdot Z$$

$$[2.22] \quad Z = \overline{((a \cdot b) \cdot d \cdot (\overline{c} + c))} = \overline{(a \cdot b \cdot d)} = \overline{a} + \overline{b} + \overline{d}$$

[2.23]

A	B	$X = \overline{A} \cdot B + A \cdot \overline{B}$	$A + B$
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	1

A	B	$Y = A \cdot B + \overline{A} \cdot \overline{B}$	$\overline{A + B}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	1	0

X = Exclusive-OR (XOR)

Y = Exclusive-NOR (XNOR)

$$Y = \overline{X}$$

[2.24]

$$f = a \cdot b + a \cdot b \cdot \overline{c} + a \cdot b \cdot c = a \cdot b \cdot (1 + \overline{c} + c) = a \cdot b$$

[2.25]

$$g = x + y + \overline{x} \cdot y + \overline{y} = x + \overline{x} \cdot y + (y + \overline{y}) \\ = x + \overline{x} \cdot y = x + y$$

[2.26]


$$J = \overline{A} \cdot B + A \cdot \overline{B} + A \cdot B + A = \overline{A} \cdot B + A \cdot (\overline{B} + B + 1) \\ = \overline{A} \cdot B + A = A + B$$

[2.27]


$$K = X + Y \cdot Z + \overline{X} \cdot Y + \overline{X} \cdot \overline{Y} = X + Y \cdot Z + \overline{X} \cdot (Y + \overline{Y}) \\ = X + Y \cdot Z + \overline{X} = (X + \overline{X}) + Y \cdot Z = Y \cdot Z$$

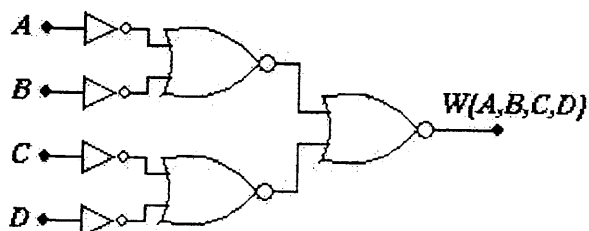[2.28]


$$W = \overline{A \cdot B \cdot C \cdot D} = \overline{A \cdot B + C \cdot D} = \overline{(\overline{A + B}) + (\overline{C + D})}$$


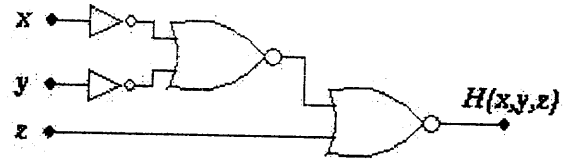
$$[2.29] \quad H = \overline{(x \cdot y) \cdot z} = \overline{x \cdot y + z} = \overline{\overline{\overline{x + y}}} + z$$



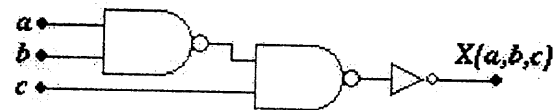
$$[2.30] \quad X = (\overline{a} + \overline{b}) \cdot c = \overline{(a \cdot b)} \cdot c = \overline{\overline{(a \cdot b)}} \cdot c$$



$$[2.31] \quad d = (a + b) \cdot \overline{b} = a \cdot \overline{b} + b \cdot \overline{b} = a \cdot \overline{b} = \overline{\overline{a \cdot \overline{b}}}$$


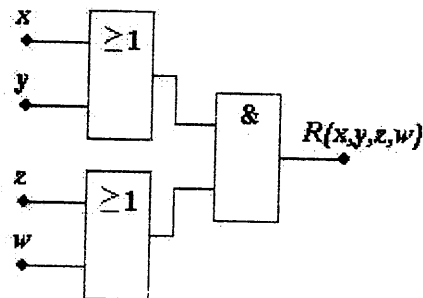
$$[2.32] \quad R = (x + y) \cdot (z + w)$$



$$[2.33] \quad f = \overline{a \cdot (b + c)} = \overline{a + (b + c)}$$

