

EE213 – Digital Systems Design

Homework 1

GNOME 2 and address decoding

NOTE: Just as on tests, I expect you to show all your work on homework problems. A correct answer with no work might not be given full credit.

1. Ch1, question 1
2. Ch1, question 4. List at least 4 features that may vary between family members. (Appendix A might be helpful).
3. For the following circuit:
 - a) What is the address space of RAM1 and ROM1?
 - b) List at least 3 locations that we could address REG1.
4. Say you are trying to hook up RAM (each chip with a standard \overline{CS}) to a microcontroller with 16 address lines (A0 through A15).
 - a) Draw a circuit which uses just 2 74LS138s (and no other parts) to create an address space for 16 4kx8 RAM chips. (Hint: There is a good reason for having multiple chip selects on the 74LS138).
 - b) Extending this model, how would you hook up 74LS138s to create separate address spaces for 8 4kx8 and 16 2kx8 RAM chips (you need only label the pins of the 74LS138s, showing what they would be connected to).
 - c) For part b), find the address space for each chip.

5. a) Write an ASM program for the GNOME which performs the same function as the code:

```
temp = 0
for i = 0 to 5
    temp = temp + i
next i
end
```

Your ASM program should also count up.

- b) Give the machine code for the first three and last three instructions (Assuming the first instruction is at code address 0).
- c) Prove your code works by showing a table of values in appropriate registers and memory locations as the program executes (like we did in class for program 3*5).
- d) For 2 extra homework points, write an ASM program which uses “for i=0 to 10” instead of “for i=0 to 5”. (You do not have to do this part. It must be correct if you want the extra credit).
6. Draw a timing diagram over a single instruction cycle showing each of the control signals in the GNOME, when the GNOME executes the instruction: `sta Rn`, which is located at memory address 42H. The control signals that should appear on your plot are: write, OE, WR, load_IR_all, load_IR_bottom, rd_data, load_PC, jump_pc, load_ACC, alu_op (assume `alu_op = 0` means do nothing), and clock. Please mark each state (fetch, decode, execute).
7. The 8051 has a command **AJMP** *addr*, where *addr* is an absolute address within the current “page”. For instance, if $PC = PC_6PC_5 \cdots PC_0$ and $addr = A_3A_2A_1A_0$, then AJMP *addr* would change the PC to $PC = PC_6PC_5PC_4A_3A_2A_1A_0$. The page is set by $PC_6PC_5PC_4$ and the address within the page by $A_3A_2A_1A_0$. (Note that for the 8051, PC and *addr* both contain several more bits, but you get the basic idea). We would like to create a similar command for the GNOME.
- a) Modify the original GNOME diagram with hardware which allows the bottom 4 bits of the PC to be loaded into the ACC.
- b) Add hardware which allows the ACC to be loaded into the bottom 4 bits of the PC.
- c) Create opcodes for the two instructions above (let’s call them “`lda_pc`” and “`ajmp_acc`”) that cannot be confused with any of the existing instruction opcodes (for instance, you cannot use the opcode 1000101 because the GNOME would interpret this as a `jmp 5`).