



CpE 213

Digital Systems Design

Lecture 3
Tuesday 9/2/2003

Basic information

- Instructor: Sahra Sedigh-Ali
 - Email: sedighali@ieee.org
 - Phone: 341-7505
 - Office: EECH 219
 - Office Hours: TR 1:30-3:00, or by appointment.
 - Email is the best way to reach me.
-

Prerequisites by Topic

- Familiarity with C programming.
- Knowledge of the functions of NAND, NOR, decoders, multiplexers, and similar combinational logic elements.
- Knowledge of the functions of D flip-flops, registers, counters, and similar sequential logic elements.

Important reminder

- The course syllabus is a legally binding agreement between you and your instructor.
- Portions have been skipped in class.
- Please read it in its entirety.


Documents you should have

- Syllabus
- Schedule
- Lecture 1 Notes
- Lecture 2 Notes
- ISM Errata
- WIMP 51 handout

Extra credit opportunity

- Get 5 (out of total 100 points)
- Come to my office (EECH219) during office hours to have your picture taken

32K memory system

 

Question 4


- What is the usual meaning of “16-bit” in the phrase “16-bit computer”?

“16-bit computer” refers to the fact the size of the data bus of the CPU is 16 lines wide.


Intro to computer organization

- Most processors today are von Neuman
 - single locus of execution
 - program and data in same storage
- Use a non-commercial 4 bit machine-GNOME2
 - Simple instruction set - 16 vs 8051's 255
 - Accumulator based architecture - like 8051
 - No input/output subsystem
 - Easy to construct from scratch in an FPGA

GNOME2 Microprocessor

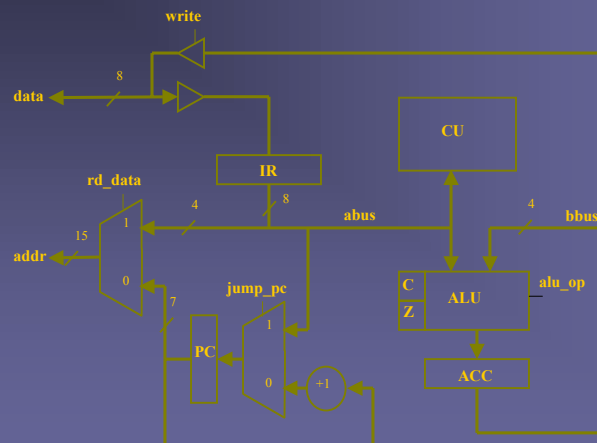


Wimp51 Microprocessor

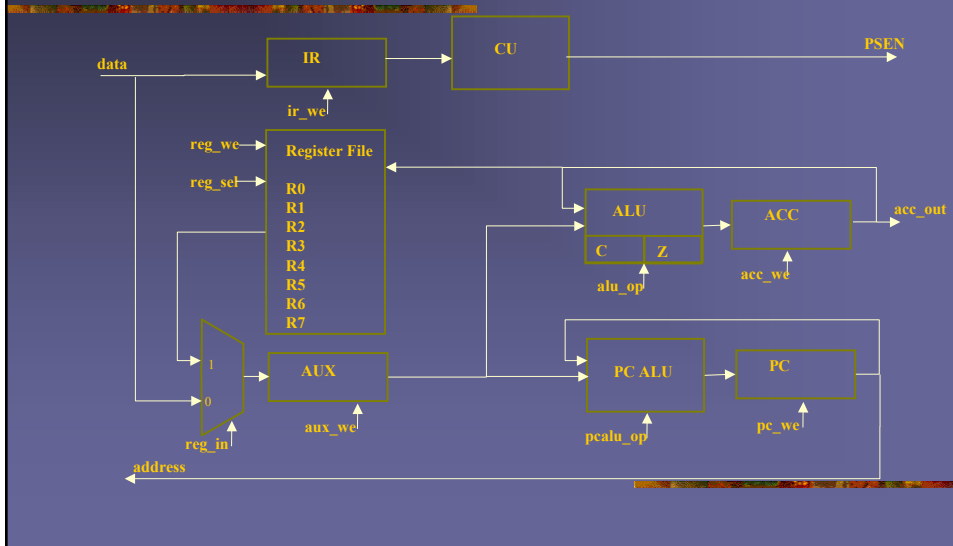


Register = array of flip flops

 
- Stack 8 flip flops to get 8 bit data register
- Strobe Clk to get $D3 \leq Q$;



Register + Logic = State machine

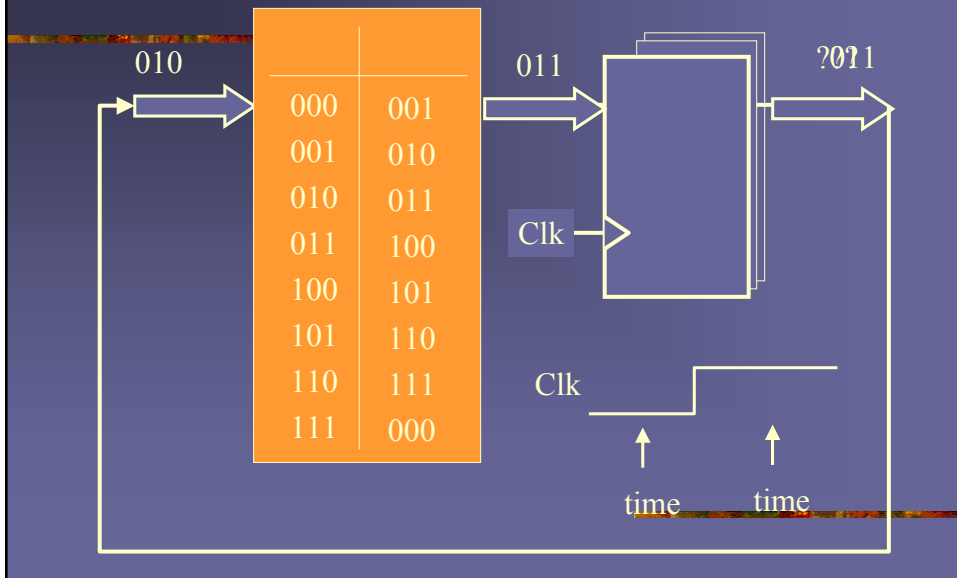

A counter!

 


Wimp51 subsystems


- PC is an eight bit counter, 0 to 255
- AUX reg can be added to PC for jump instr
- ACC and ALU form a 'register with logic' block
- IR and memory form a 'register with logic' block
- Control Unit (CU) is a 2 bit counter, 0 to 2
- Datapath = IR, AUX, PC, ACC, Regfile, ALU, PCALU
 - 12 registers plus Logic (ALU, PCALU)

Wimp51 control unit

 
- Simple state machine
- Fetch/Decode/Execute states
- Each state takes one clock cycle
- A complete loop is an instruction cycle




Wimp51 control unit

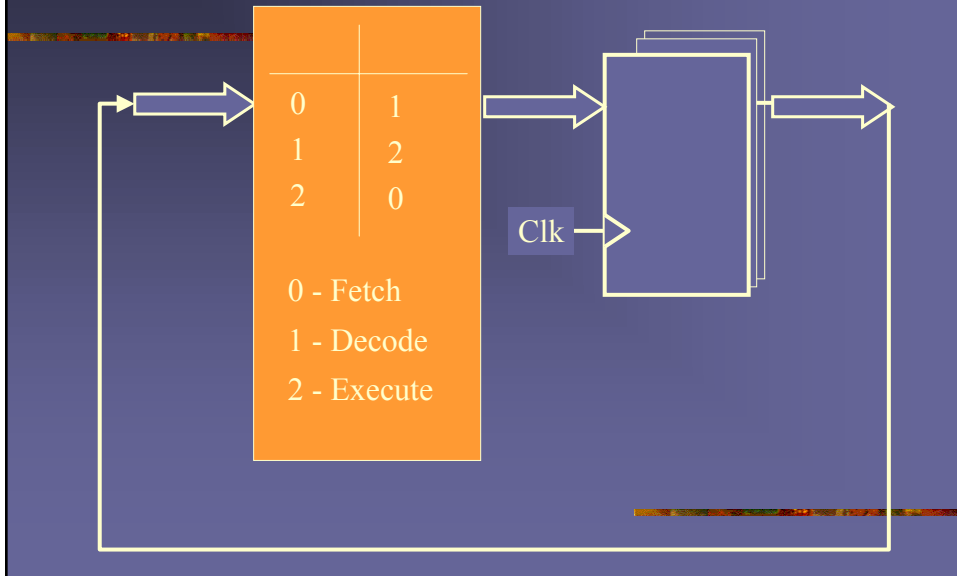

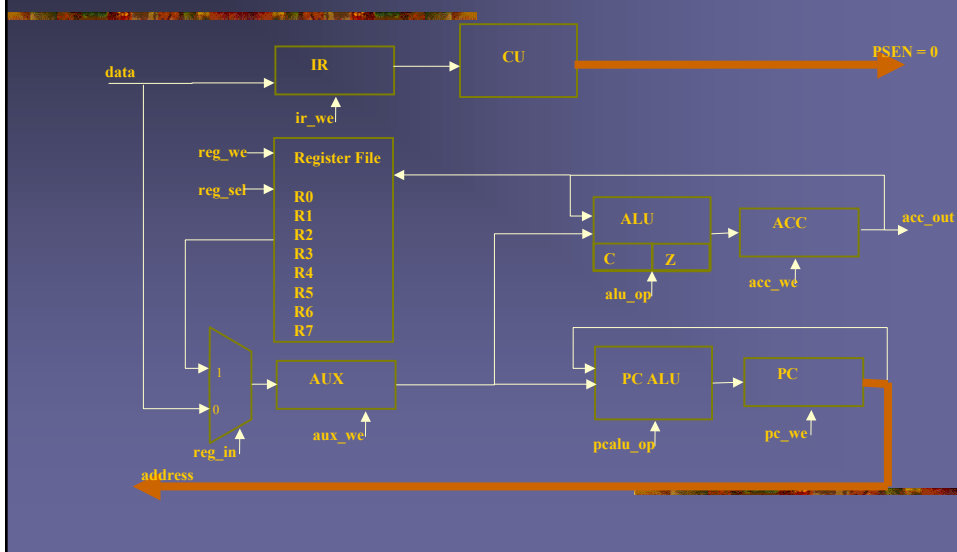
Fetch cycle step 1: $\text{addr} \leq \text{PC}$



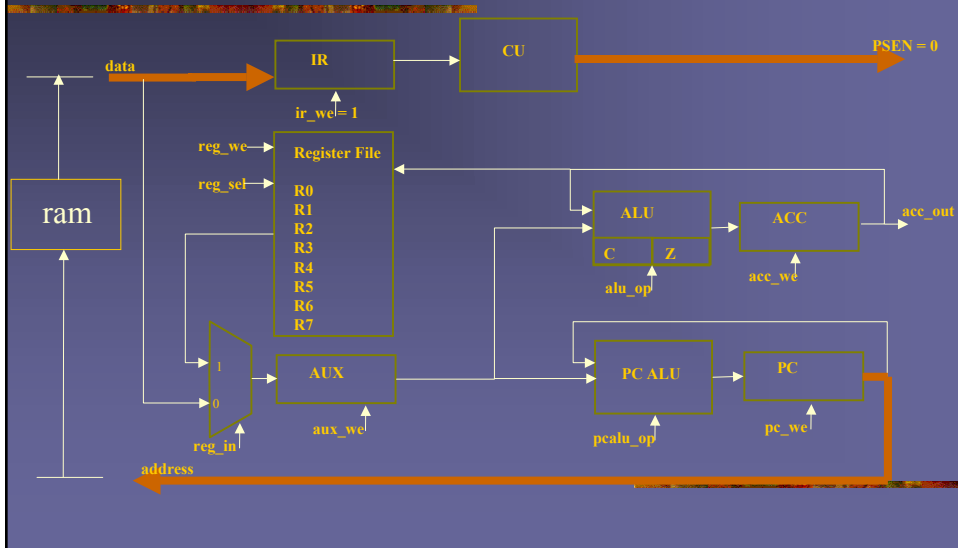Fetch cycle step 2: $IR \leq \text{data}$



Fetch cycle: $PC \leq PC + 1$

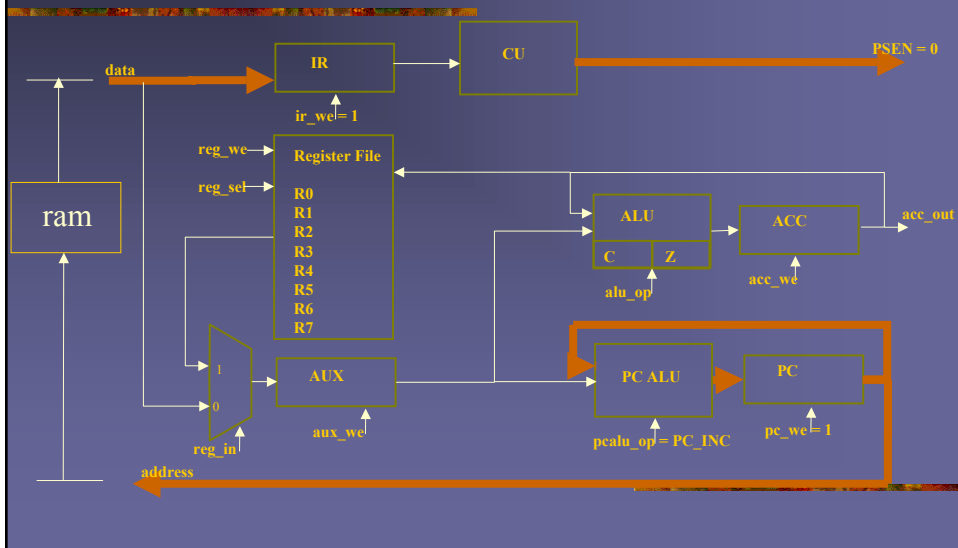

Before the next lecture

- Review WIMP handout
- Finalize four partners that you will work with for the rest of the semester
- Answer questions from WIMP handouts
- Bring your answers to class for discussion