

Cp Eng 111, Section P
Fall 1999

Final Exam

Name: Jessie Wu
12/14/99

200
fantastic!

Show all work on the exam papers. If you need additional space, use the reverse side of the paper. Closed book, closed notes, no calculator.

1. (a) Convert ^{428.12}101.01 from binary to decimal equivalent.
(20) $\frac{1}{2^2}$ $4 + 1 + \frac{1}{2^2} = 5 + \frac{1}{4} = \boxed{5.25}$

- (b) Convert the decimal number 19.75 to binary.

$$\begin{array}{l|l} 19 = 9 & r_0 = 1 \\ 9 = 4 & r_1 = 1 \\ 4 = 2 & r_2 = 0 \\ 2 = 1 & r_3 = 0 \\ 1 = 0 & r_4 = 1 \end{array} \quad \begin{array}{l} .75 \cdot 2 = 1.5 \quad r_{-1} = 1 \\ .5 \cdot 2 = 1 \quad r_{-2} = 1 \end{array}$$

$$\boxed{10011.11}$$

- (c) Convert 0x4F to decimal

$$64 + 15 = \boxed{79}$$

- (d) What is the 8-bit 1's complement of 10000010?

$$\boxed{01111101}$$

- (e) What is the 8-bit 2's complement of 10100000?

$$\begin{array}{r} 01011111 \\ + 00000001 \\ \hline 01100000 \end{array}$$

$$\boxed{01100000}$$

$$01011111 \quad \checkmark$$

$$01100000 \quad -0$$

2. Determine whether each of the following is True (T) or False (F). Circle the appropriate choice.

(a) NOT and AND form a complete logic set.

T F

(b) AND and OR form a complete logic set.

T F

(c) $A + \bar{A}B = A + B$

T F

(e) If a sequential network has a 4-state transition diagram, it will take 4 memory elements to implement its design.

T F

(e) If a sequential network has a 7-state transition diagram, it will take 3 memory elements to implement its design.

T F

(f) A 4:1 MUX has 2 select (input) lines.

T F

3. Given the truth table below,


(14) (a) Complete the truth table, for the function $f(x,y,z) = (x + \bar{y}) \cdot z$

$x + \bar{y}$	\bar{y}	x	y	z	f(x,y,z)	g(x,y,z)
1	1	0	0	0	0	0
1	1	0	0	1	0	0
0	0	0	1	0	0	1
0	0	0	1	1	0	0
1	1	1	0	0	1	1
1	1	1	0	1	1	1
1	0	1	1	0	0	0
1	0	1	1	1	1	0

(b) Write $g(x,y,z)$ as a canonical sum of products.

$$g(x,y,z) = \bar{x}y\bar{z} + x\bar{y}\bar{z} + x\bar{y}z$$

 
4. Construct the VHDL listing that describes the logic circuit shown below:
(15)



entity problem-4 is
port (a,b,c : in bit;
F : out bit);
end problem-4;

architecture Logic of problem-4 is
begin
F <= (b nand c) xnor not(a);
end Logic;

 5. Given the following CMOS circuit, determine the function $g(x, y, z)$.
(15)



nor

p fets in parallel NAND

x	y	z	g	y+z	(y+z)*x
0	0	0	1	0	0
0	0	1	1	1	0
0	1	0	1	1	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	0	1	1

$\overline{X} \cdot \overline{Y} + Z$ p fets series
n fets parallel

$$\overline{Y+Z} + \overline{X}$$

$$Y+Z = X$$

~~0~~

6. For the circuit below, calculate the propagation delay between the NAND gate and output 2, given the following parameters and assuming that both outputs drive an inverter.

$$t_{p0, \text{NOT}} = 0.5 \text{ ns}$$


$$t_{pL, \text{NOT}} = 0.4 \text{ ns}$$

$$t_{p0, \text{NAND}} = 0.85 \text{ ns}$$

$$t_{pL, \text{NAND}} = 0.95 \text{ ns}$$

$$t_{p0, \text{NOR}} = 0.8 \text{ ns}$$

$$t_{pL, \text{NOR}} = 0.9 \text{ ns}$$

 

$$t_{p0, \text{NAND}} + t_{pL, \text{NOT}} + t_{pL, \text{NOR}} + t_{p0, \text{NOR}} + t_{pL, \text{NOT}} = 0.85 + 0.4 + 0.9 + 0.8 + 0.4 = 3.35 \text{ ns}$$

$$\begin{array}{r} 1.6 \\ 1.75 \\ \hline 3.35 \end{array}$$

7. For each of the following, consider an 8-bit register whose initial value is 10001111. Assume this initial state for each operation below; determine the contents of the register after each operation.

(a) SHL 1

00011110

10001111

(b) ROR 2

11100011

10001111

$$\begin{array}{r} 0.85 \\ 0.8 \\ \hline 1.65 \\ 2.15 \\ \hline 3.05 \end{array}$$

✓
-0

8. (a) Generate the Karnaugh map for $f(x,y,z) = \sum m(0, 1, 2, 5, 6)$

yz

x \ yz	00	01	11	10
0	1	1	1	1
1	1	1	0	1

000
001
010
101
110

- (b) Find the simplest form of the function $g(w, x, y, z)$ which is described by the following K-map:

zw \ xy	11	10	00	01
01	1	1	0	1
11	1	1	0	0
10	1	0	0	0
00	0	1	0	1


$$g(w, x, y, z) = yz + xzw + \bar{x}z\bar{w} + \bar{x}\bar{z}w$$

✓
-0

9. Given the following state transition table,
(20)

	x	
	0	1
A	D/0	B/0
B	C/0	D/0
C	B/0	C/0
D	B/0	C/1

 - (a) Draw the corresponding state transition diagram



- (b) Assuming you start at state A, determine the output sequence for the following input sequence: 00111101
1 2 3 4 5 6 7 8

00010000

000/0000

at A

1	out 0	at D
2	out 0	at B
3	out 0	at D
4	out 1	at C
5	out 0	at C
6	out 0	at C
7	out 0	at B
8	out 0	at D

10. Multiple choice (circle the correct answer):
(10)

(a) The transmission gate network below implements which of the following functions?

~~A OR B~~


~~A OR NOT B~~

~~A XOR B~~

A XNOR B

A	B	
0	0	1
0	1	0
1	0	0
1	1	1

$A \text{ xnor } B$

 

$$ab + \bar{a}\bar{b}$$

(b) The MUX below implements which of the following functions?

A OR B


A OR NOT B

A XOR B

A XNOR B

b	a	
0	0	0
0	1	1
1	0	1
1	1	0


$A \text{ xor } B$

 

✓
0


11. Draw the state transition diagram for a 3-bit odd parity network, that is, the output should be 0 unless the third input yields a 3-bit sequence with odd parity; in this case, the output should be 1. In all events, the system should return to its initial state after the third input bit.

3 bit odd parity check
out = 0

 

12. Use an 8:1 MUX to implement the function $F(A, B, C) = A \cdot B \cdot C + B \cdot \bar{C}$
(10)

A	B	C	\bar{C}	$B \cdot \bar{C}$	$A \cdot B \cdot C$	F
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	1	0	1	1	0	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	0	0	0
1	1	0	1	1	0	1
1	1	1	0	0	1	1

 

A	B	C	$A \cdot B \cdot C$	\bar{C}	$B \cdot \bar{C}$	F
0	0	0	0	1	0	0
0	0	1	0	0	0	0
0	1	0	0	1	1	1
0	1	1	0	0	0	0
1	0	0	0	1	0	0
1	0	1	0	0	0	0
1	1	0	0	1	1	1
1	1	1	1	0	0	1

13. Complete the timing diagram below for a positive edge-triggered D flip-flop, assuming an initial value of 0 for Q.
(15)

